

# 2's complement

unsigned 4-bit number  
 0-15  $\in 2^4 = 16 \rightarrow$

$$(2^3 - 1) + (-2^3) = 7, 6, 5, \dots, 0, \dots, -7, -8.$$



3 + (-5)

0	0	1	1	+3
1	0	1	1	-5
1 1 1 0				-2 ✓

6 + (-2)


0	1	1	0	
1	1	1	0	
0 1 0 0				✓

Adders

→ one Bit Half Adder  
→ one bit full Adder

X	Y	Z	Count
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Count (carry)

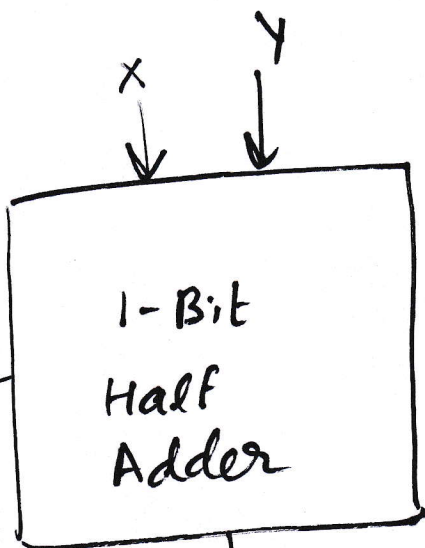



→ Logic to add 1-bit, 2-bit, 4-bit, 8-bit, .... remains the same

→ Only diff. is that circuit becomes bigger

Z (Sum)

$$Z = X \cdot \bar{Y} + \bar{X} \cdot Y$$

$$\text{Count} = X \cdot Y$$

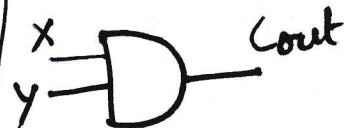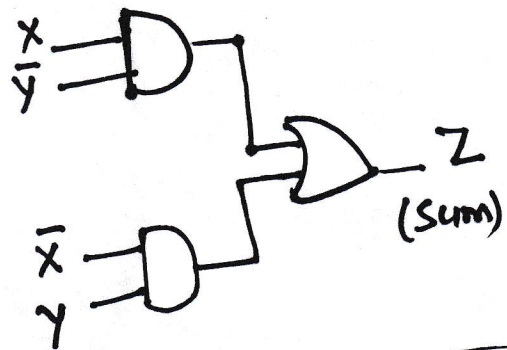

$$\begin{array}{r} 3 \quad 0011 \\ + 4 \quad 0100 \\ \hline 7 \quad 0111 \end{array}$$

$$\begin{array}{r} 0011 \\ + 0010 \\ \hline 0101 \end{array}$$


$$\begin{array}{r} 0100 \\ + 0001 \\ \hline 0101 \end{array}$$

$$\begin{array}{r} 1 \\ 0 \\ \hline \end{array}$$

$$\begin{array}{r} 0101 \\ + 0101 \\ \hline 1010 \end{array}$$

# One-bit Full Adder

(carry)  
out

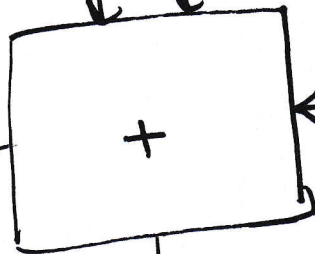


Cin  
0


Z (sum)

$$Z = X \cdot Y \cdot C_{in} + X \cdot \bar{Y} \cdot \bar{C}_{in} + \bar{X} \cdot Y \cdot \bar{C}_{in} + \bar{X} \cdot \bar{Y} \cdot C_{in}$$
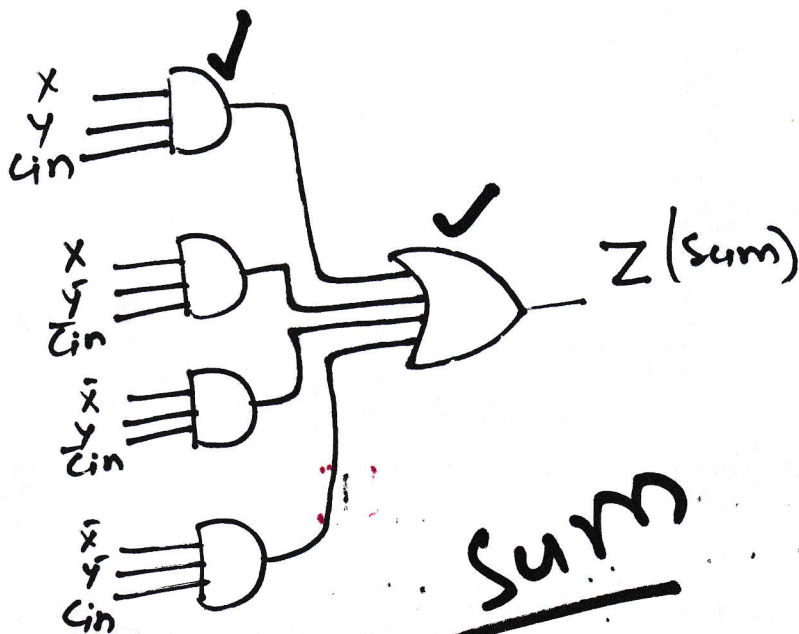
$$C_{out} = X \cdot Y + X \cdot C_{in} + Y \cdot C_{in}$$



sum

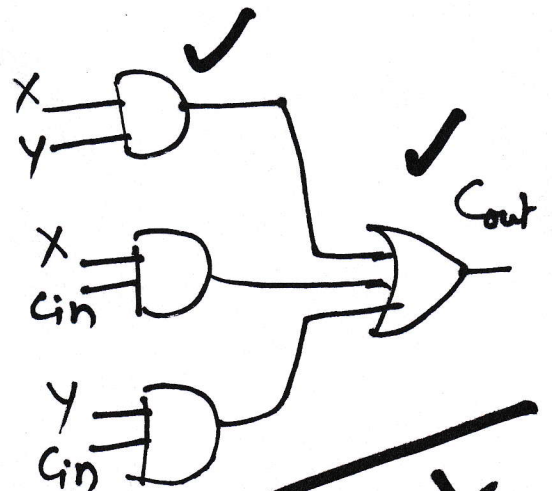


carry



①

4-bit adder -	4 steps	4 ✓	Processor cycle
8-bit adder -	8 steps	8 ✓	
16-bit adder -	16 "	16 ✓	
32-bit adder -	32 "	32	
64-bit adder -	64 "	64 ✓	very big

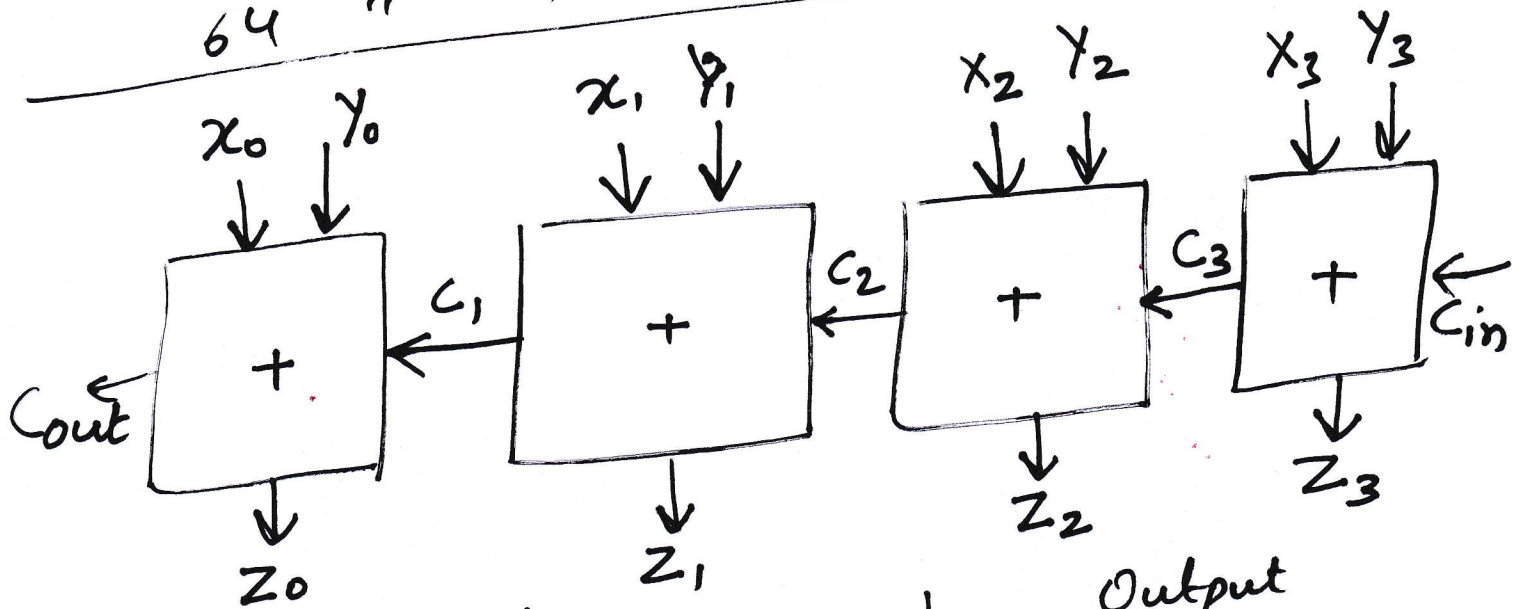

Input

$$X = X_0 X_1 X_2 X_3$$


$$Y = Y_0 Y_1 Y_2 Y_3$$

$C_{in} \rightarrow$  Initially zero

Output  
 $Z = Z_0 Z_1 Z_2 Z_3$   
 $C_{out}$

$\boxed{+}$   $\rightarrow$  one bit full adder.

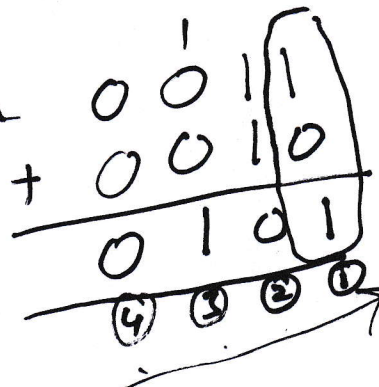$\rightarrow$  3) also serial adder  
 4) slow adder




1) Carry is riddled from one stage to the other  
 2) Ripple-carry

2

# Parallel Adder

1

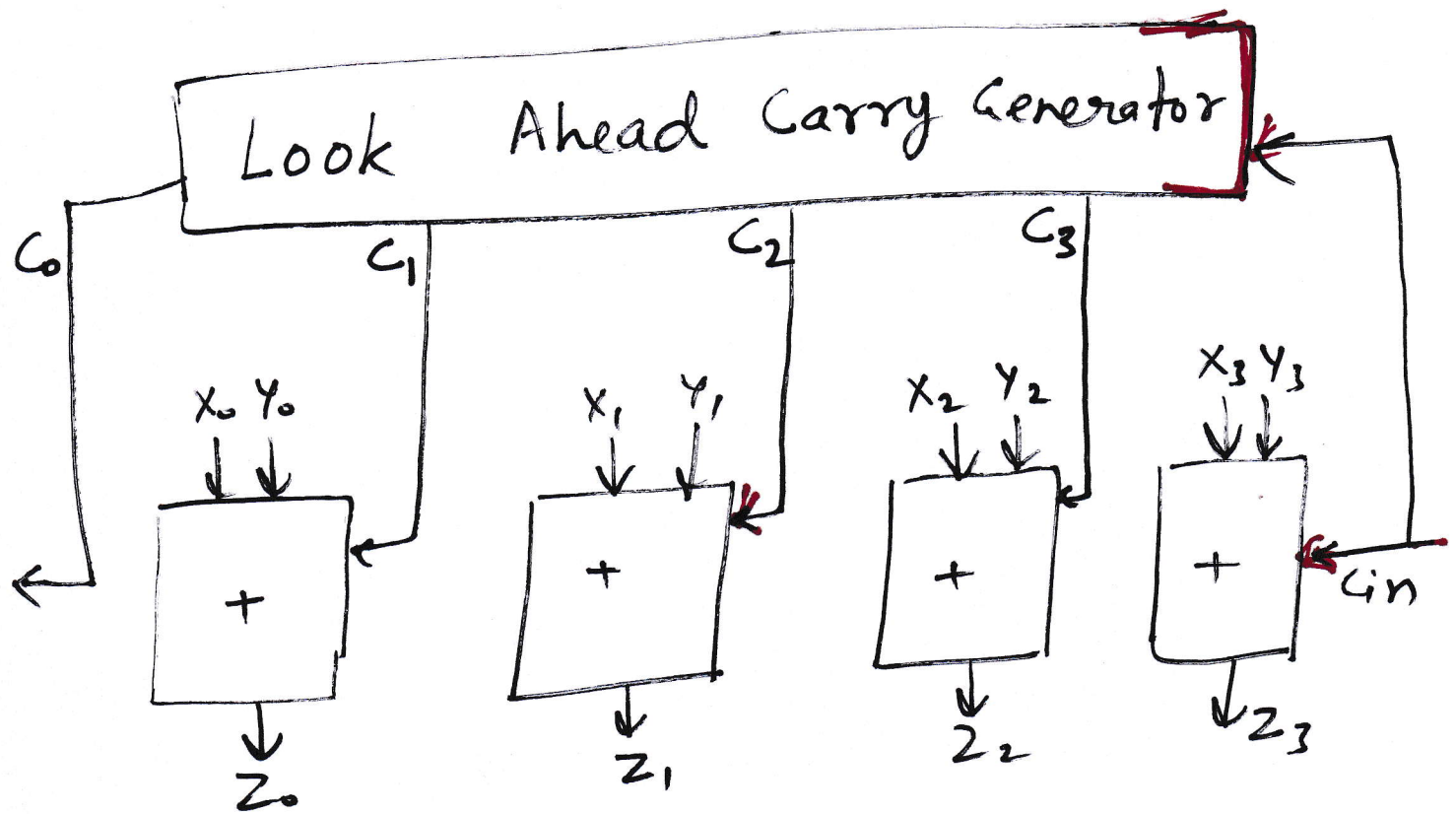

③

$$C = X \cdot Y + X \cdot C_{in} + Y \cdot C_{in}$$

②

$$C_3 = \underbrace{X_3 \cdot Y_3} + X_3 \cdot C_{in} + Y_3 \cdot C_{in}$$

$$C_3 = \underbrace{X_3 \cdot Y_3} + C_{in} \cdot \underbrace{(X_3 + Y_3)}_{p_3}$$

generate  $\leftarrow g_3$  $p_3$   $\rightarrow$  propagate

$$C_3 = g_3 + p_3 \cdot C_{in} \quad \text{--- ①}$$

$$C_2 = g_2 + p_2 \cdot C_3$$

$$\Rightarrow C_2 = g_2 + p_2 g_3 + p_2 p_3 C_{in} \quad \text{--- ②}$$

$$C_1 = g_1 + p_1 \cdot C_2$$

$$C_1 = g_1 + p_1 g_2 + p_1 p_2 g_3 + p_1 p_2 p_3 C_{in} \quad \text{--- ③}$$


$$C_0 = g_0 + p_0 C_1$$

$$C_0 = g_0 + p_0 g_1 + p_0 p_1 g_2 + p_0 p_1 p_2 g_3 + p_0 p_1 p_2 p_3 C_{in}$$

(4)

(3)

## Parallel Adder

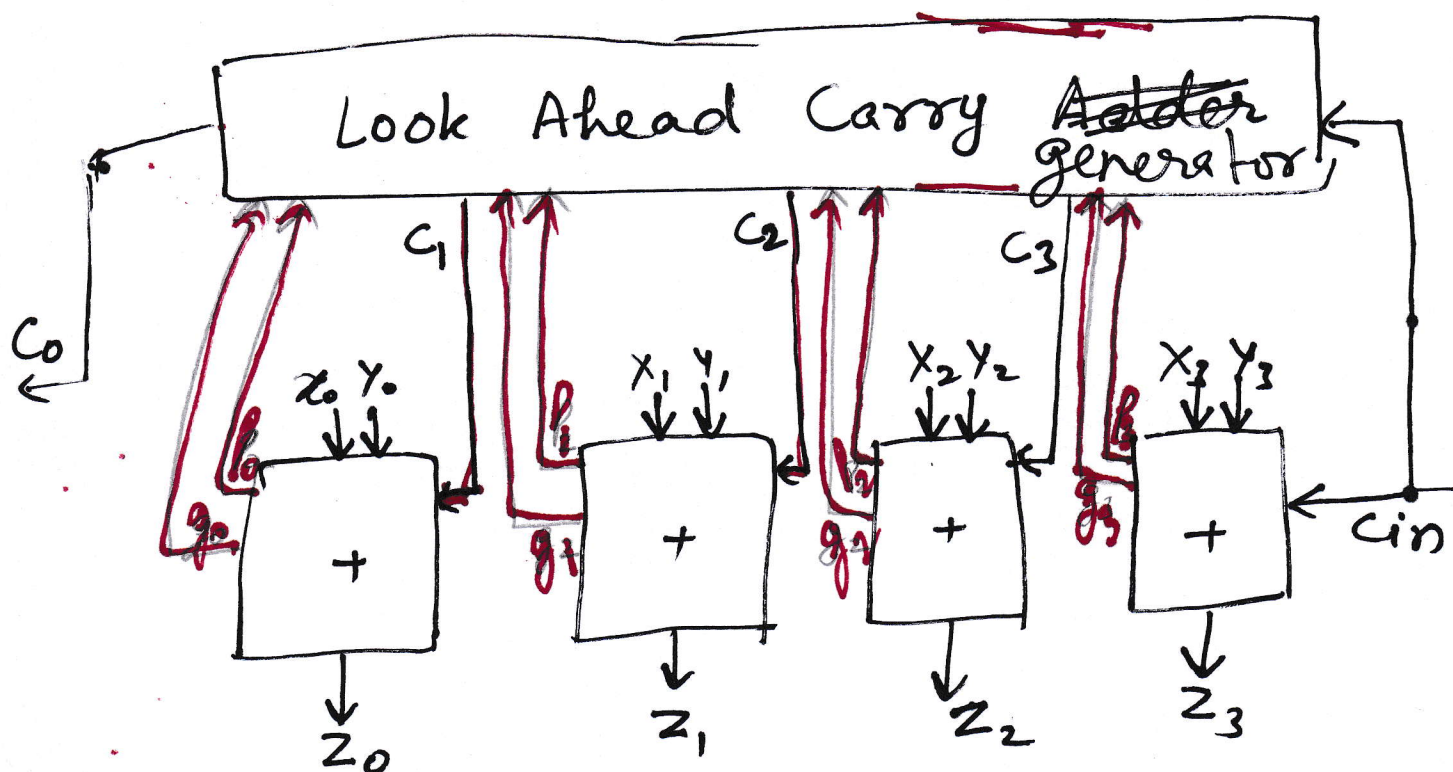

→ We will predict (look ahead) all the carry.

→ Using all  $X$ -bits,  $Y$ -bits, and  $C_{in}$ , we will predict  $C_3, C_2, C_1, C_0$  [out]

→ This should be done in



⑤

→ All work done in just 3 cycle

→ ~~once~~ One cycle will produce all g's & p's.

→ One cycle will produce all carries independently using g's, p's, and  $C_{in}$ .

→ Last cycle, ~~all~~ all the adder circuits will produce the result.



6


# Subtraction :

$$X - Y$$

$$= X + (2's \text{ complement of } Y)$$

$$= X + (1's \text{ complement } Y + 1)$$

$$= X + (Y' + 1)$$

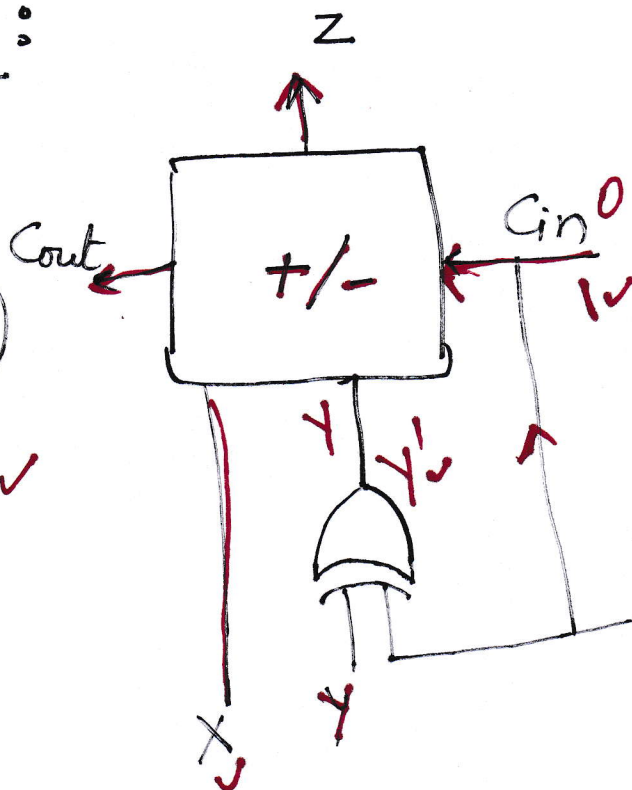

$$S = \begin{matrix} X + Y \\ X - Y \end{matrix}$$

	XOR		
$s=0$	0	0	0
	0	1	1
$s=1$	1	0	1
	1	1	0